

# EE210: Analog Electronics

## Question Set 3

Instructor: Imon Mondal, imon@iitk.ac.in

1) : Sketch the two port incremental Y-Parameter for the network shown in the figure with the following I-V characteristics.

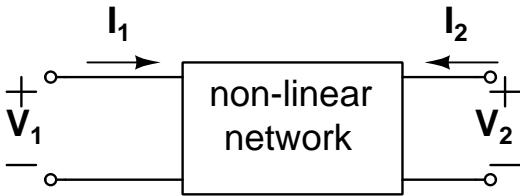


Fig. 1. Problem 1

a) :  $I_1 = 0$  for all  $V_1, V_2$ .

$$I_2 = \begin{cases} \beta V_1^2 & \text{when } V_1 \geq 0 \\ 0 & \text{otherwise.} \end{cases}$$

b) :  $I_1 = 0$  for all  $V_1, V_2$ .

$$I_2 = \begin{cases} \beta(V_1 - V_{th})^2 & \text{when } V_1 \geq V_{th} \\ 0 & \text{otherwise.} \end{cases}$$

c) :  $I_1 = 0$  for all  $V_1, V_2$ .

$$I_2 = \begin{cases} \beta(V_1 - V_{th})^2(1 + \lambda V_2) & \text{when } V_1 \geq V_{th} \\ 0 & \text{otherwise.} \end{cases}$$

d) :  $I_1 = I_2 / (\beta)$  for all  $V_1, V_2$ .

$$I_2 = I_o e^{v_1/v_T} \text{ for all } V_1, V_2.$$

2) : Find  $v_o/v_i$  if the incremental two port network has Y-Parameters corresponding to Q1 (a-d)

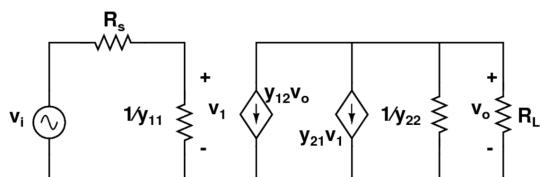


Fig. 2. Problem 2

3) : Find the following

a) : Find  $v_o/v_i$ .

b) : Find  $v_o/v_i$  when  $y_{21} \rightarrow \infty$ .

c) : Find  $v_o/v_i$  when  $R_L \rightarrow \infty$ .

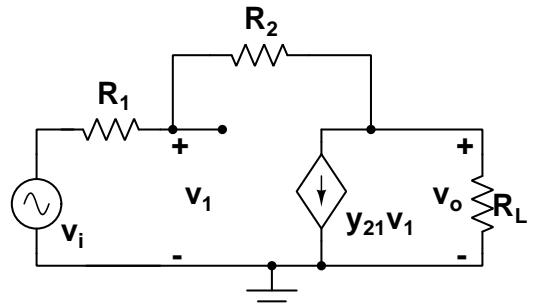


Fig. 3. Problem 3

4) : I-V characteristic of the two port network is as follows

$I_1 = 0$  for all  $V_1, V_2$ .

$$I_2 = \begin{cases} \beta V_1^2 & \text{when } V_1 > 0 \text{ and } V_2 > 0 \\ \text{in-valid} & \text{otherwise.} \end{cases}$$

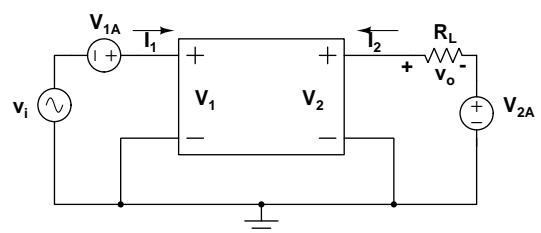


Fig. 4. Problem 4

a) : Sketch the small signal network. Assume  $V_{1A} = 1V, V_{2A} = 5V, \beta = 1mA/V^2, R_L = 2k\Omega$ .

b) : Find the small signal gain  $v_o/v_i$ .

c) : Will the small signal parameter will change if  $V_{2A} = 1V$ ?

d) : A designer wants to achieve a voltage gain of  $|v_o/v_i| = 10$  using  $R_L = 2k\Omega$ . Suggest a solution which helps her achieve the goal. You are free to change  $V_{1A}$  and  $V_{2A}$ .