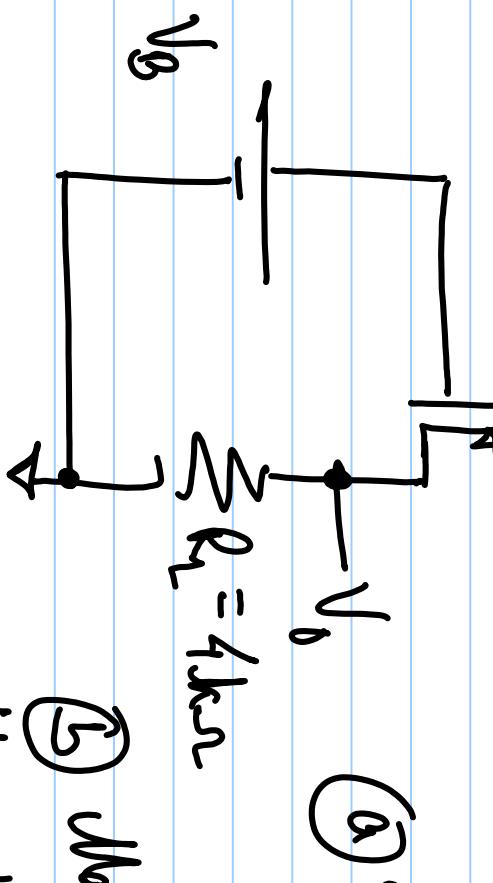


Question Set #5

①

$$V_{DD} = 5V$$

$$\text{Assume } \mu_0 C_o r \frac{W}{L} = 2mk / V^2, \quad V_{thp} = 1V$$




② Plot V_o with respect to V_B
if V_B is varied from 0 to 5V.

③ Mark all regions of operation in
the plot.

④ Mark the regions the plot where $|slope| > 1$.
What does this signify?

②
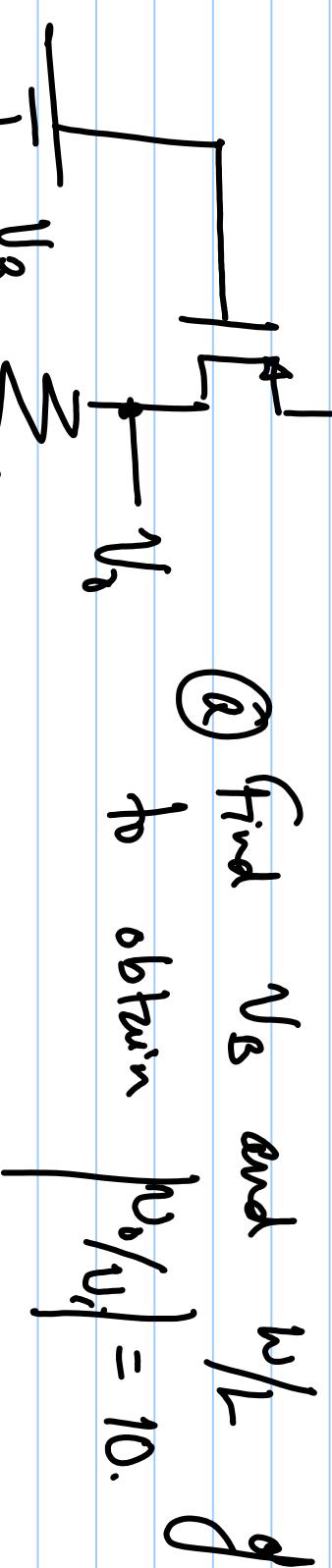
$$V_{DS} = 5V \quad \mu_{FET} = 100\mu A/V^2, \quad V_{THP} = 1V$$



ⓐ find V_B and w/L of the transistor
to obtain $\left|\mu_v/v_i\right| = 10$.

ⓑ Is the solution unique?

ⓒ Assume that we need to keep

$$\text{a minimum Overdrive Voltage, } V_{ov} = V_{SD} - V_{THP} = 100mV,$$

and maintain a small-signed gain of -10.


If $V_i = V_p \sin(\omega_0 t)$, find a V_B and w/L

such that the transistor is always in saturation
for a $V_f = 100\text{mV}$.


(3)



Sketch the "small-signal" Norton's equivalent network for the following networks. Assume that the transistors are biased in saturation. Also represent y_m of the MOSFET as γ_m . (To avoid confusion between y_m of the network, and y_m of a transistor). Find V_o/V_i for all cases.

(a)

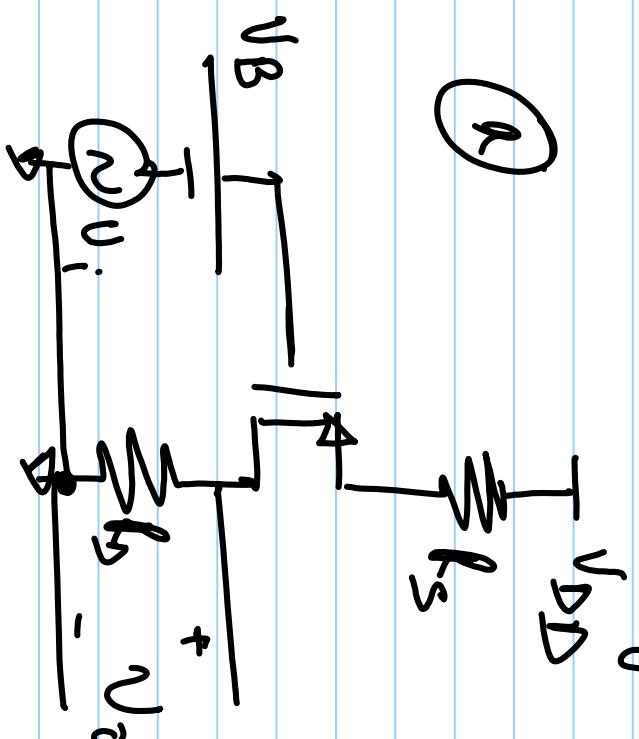

(b)

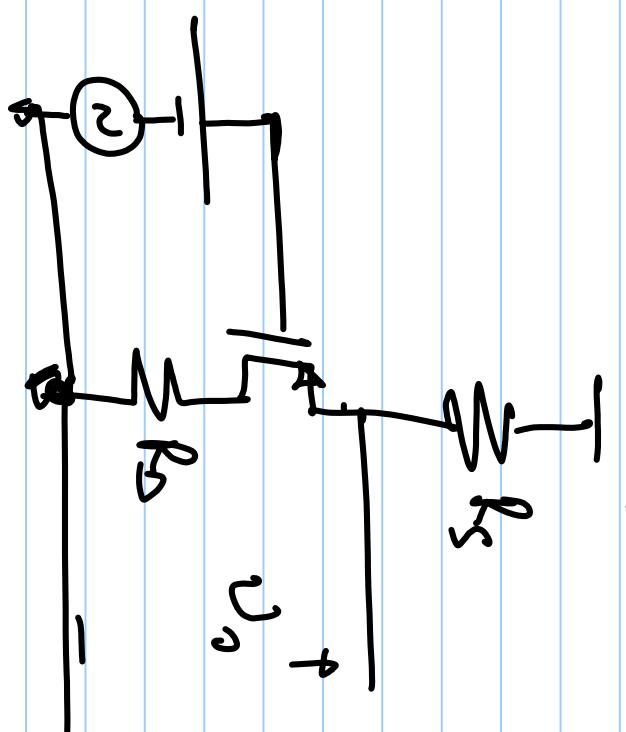

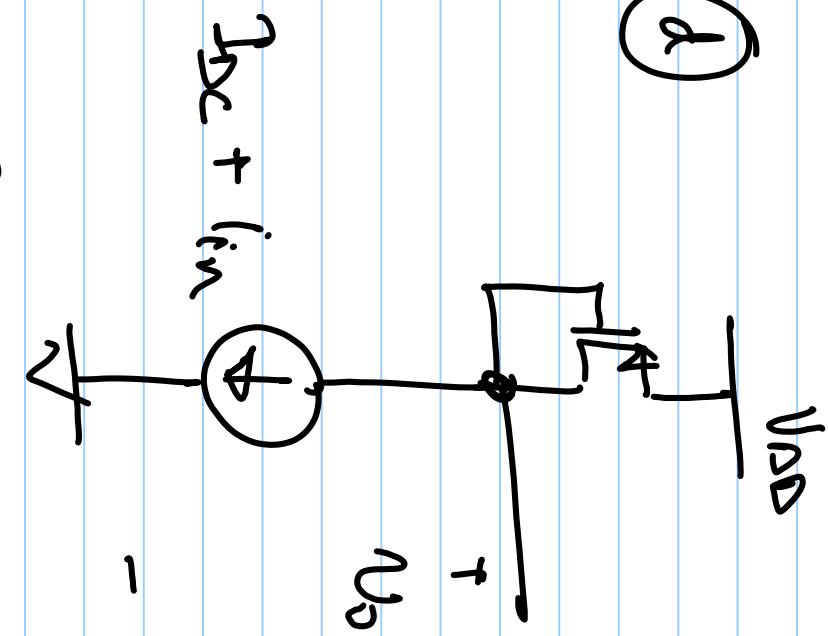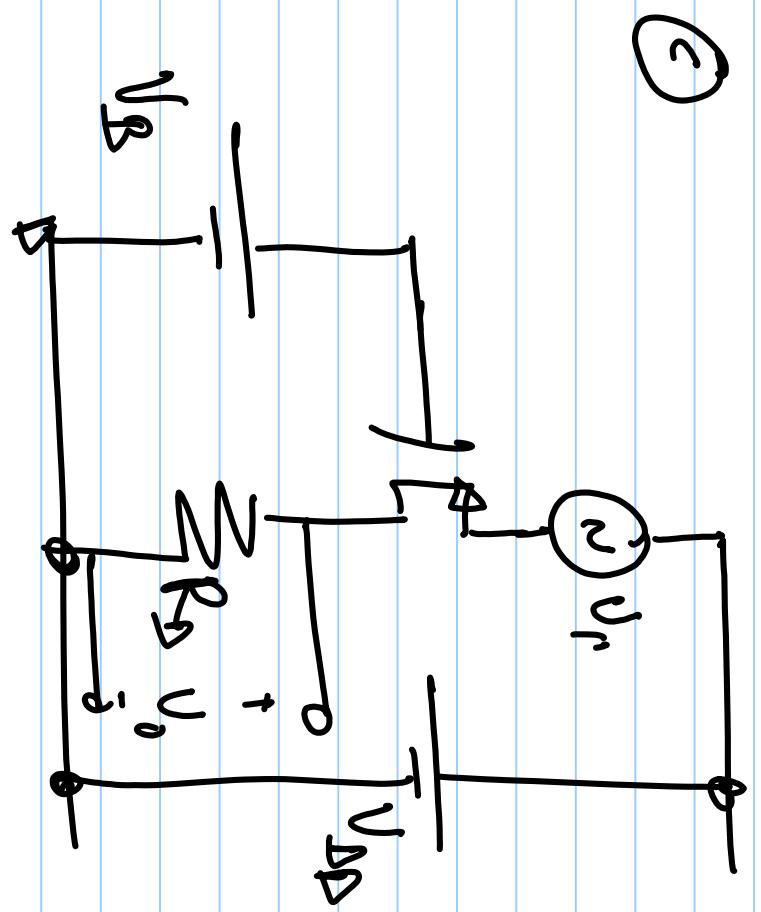

find v_o/i_{in} in this case

④

$$V_{DD} = 5V$$

$$R_g = 3.7k\Omega$$


$$n_L = 20$$

$$\mu_p C_{ox} = 100 \mu A/V^2$$

$$V_{mp} = N$$

(a) find V_B such that

$$V_o = V_{DD} - V_{BG}$$

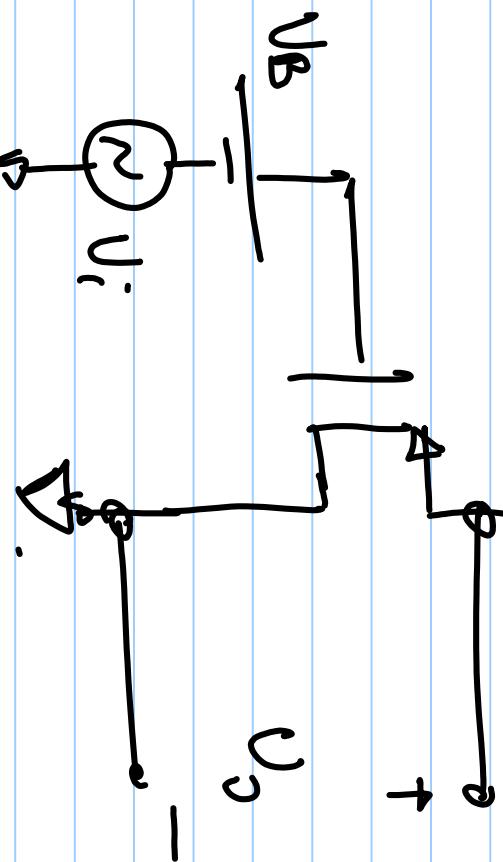

(b) find V_o / V_i .

c) If $V_i = V_p \sin(\omega t)$, what is the max V_o that you can apply while keeping the transistor in saturation and keeping $V_{ov} \geq 100mV$.