

Question Set #6


①

A designer aims to realise a gain of -200 using a common source amplifier. She has a battery of $3V$ and a MOSFET having $\mu_{n,\text{ox}} = 0.2 \text{ mA/V}^2$ and $V_{th} = 1V$. The only constraint that she needs to follow is that

$$V_{DD} = V_{GS} - V_{th} \quad \text{must} \quad \boxed{\text{at least}} \quad \text{be } 100\text{mV}.$$

T_{VDD}

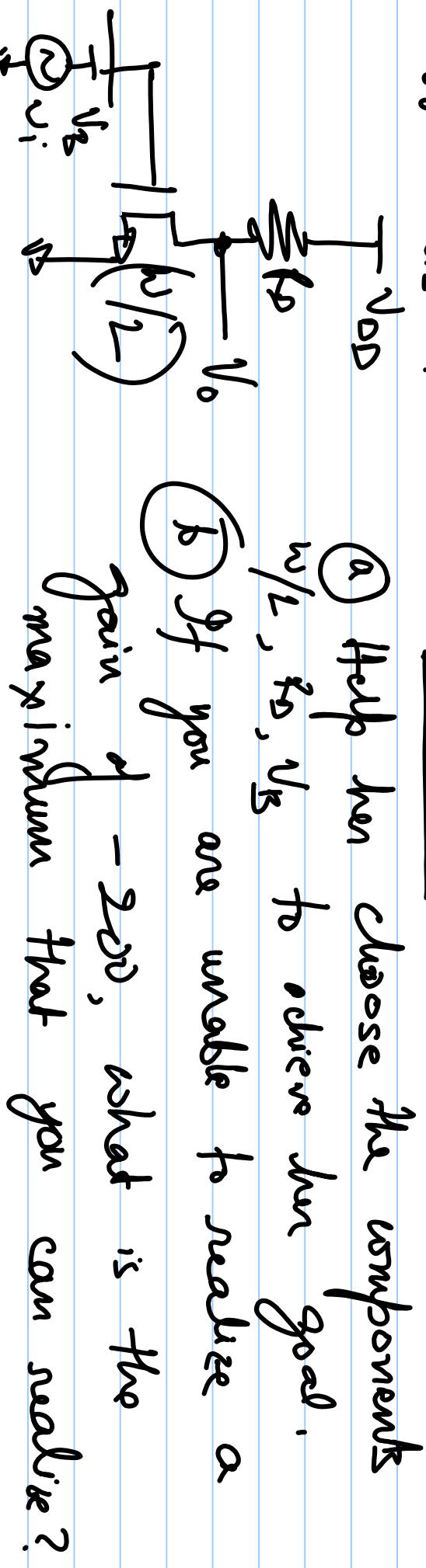a) Help her choose the components
 w/L , R_D , V_B to achieve her goal.




c) Can you improve the gain if you are allowed to pick another transistor with a different μ_{FE} ?

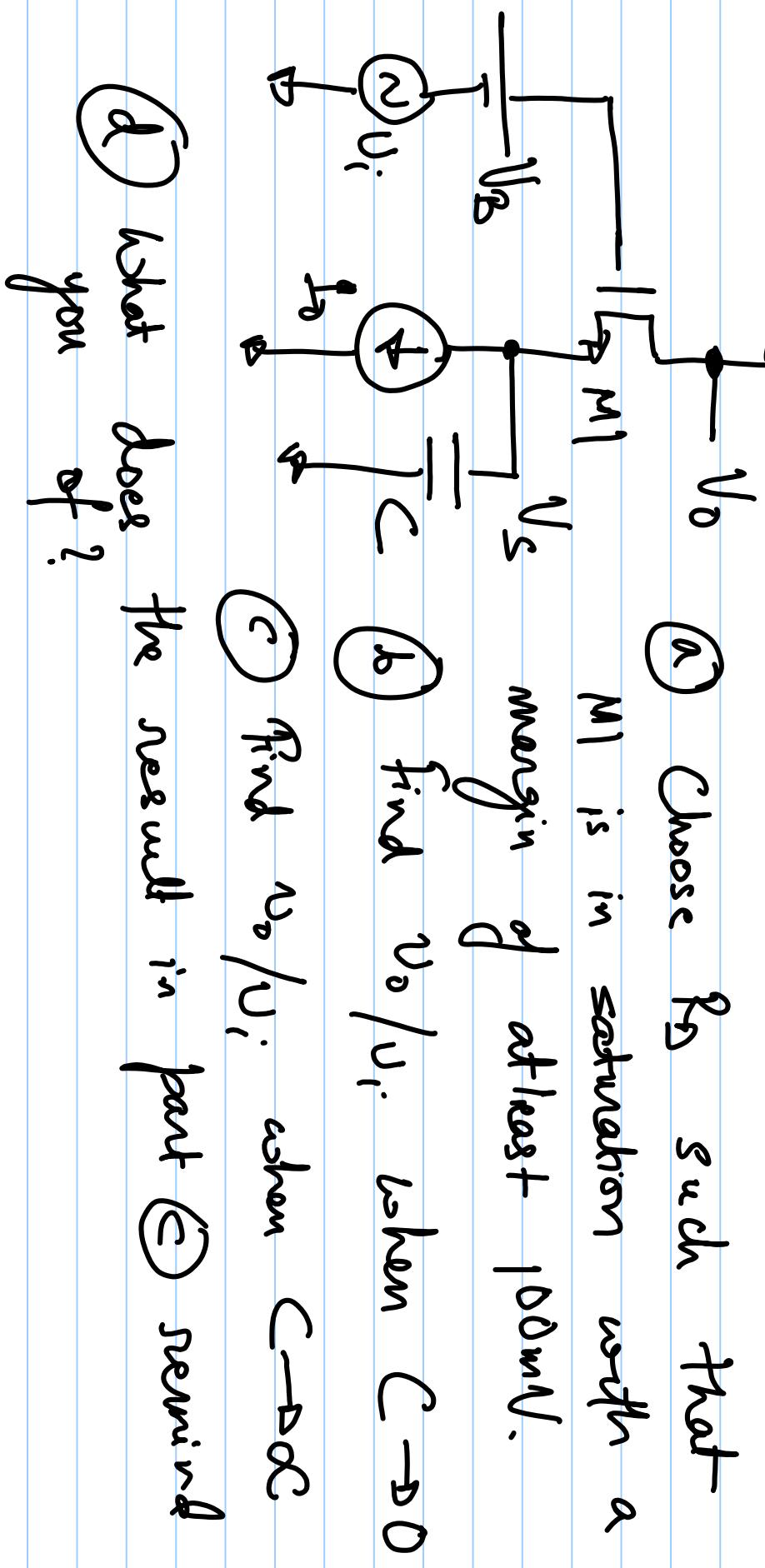d) Can you improve the gain if you are allowed to change V_{DD} ?

②

$$V_{DD} = 5V, \mu_n Lop \frac{W}{L} = 200 \mu A/V^2$$
$$V_B = 3V, I_0 = 1mA, V_{thn} = 1V$$



① Choose R_D such that

$|M|$ is in saturation with a margin of at least 100mV.

② find V_o / V_i when $C \rightarrow 0$

③ Find V_o / V_i when $C \rightarrow \infty$

d) what does the result in part (c) remind you of?

(e)

Plot $\left| \frac{V_o(j\omega)}{V_i(j\omega)} \right|$ using Bode approximation with

the corner frequencies clearly marked.

Why does the plot @ $\omega=0$ and $\omega=\infty$ make sense?

(f)

What is the time constant associated with the capacitor?


(g) Plot $\left| \frac{V_s(j\omega)}{V_i(j\omega)} \right|$ using Bode approximation.

Why does the values at $\omega=0$ and $\omega=\infty$ make sense?

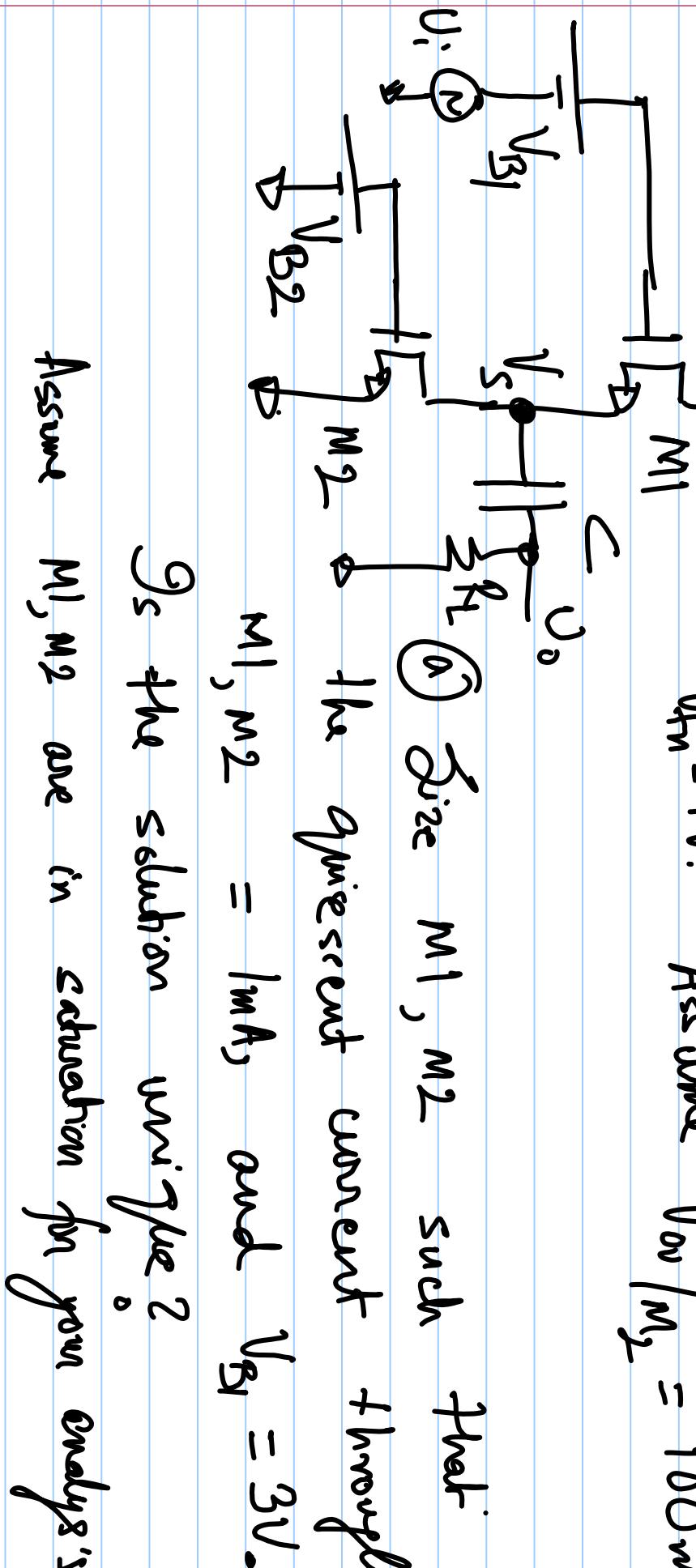(3)

$$V_{DD} = 5V \cdot \mu_n \text{ or } = 200 \mu A / V^2.$$

$$V_{in} = 1V. \quad \text{Assume } V_{ov}/M_2 = 100mV$$



(b) If $\left(\frac{w}{l}\right)_{m_1} = 10$, what is N_B/m_1 ?

c) what is the minimum N_B that \mathcal{I} can set while keeping m_1, m_2 in saturation?

(d) what changes can \mathcal{I} do to m_1 so that the minimum N_B reduces further by 200 m^2 ?

(e)

Assume $C \rightarrow \infty$, $R_L = 10k\Omega$, $V_{B1} = 3 \text{ V}$,

$$\left(\frac{w}{L}\right)_{M_1} = 10 \quad \text{for this part.}$$

If $V_i(t) = V_p \sin(\omega t)$, find the max (V_p) while keeping both transistors in saturation.

(f)

For this part assume $C = 10\text{pF}$, $R_L = 10\text{k}\Omega$,
 $V_B = 3V$, and $\left(\frac{w}{l_2}\right)_{n_1} = 10$.

$$v_i(t) = 10mV u(t) \quad [\text{where } u(t) \text{ is an unit step}]$$

Find $v_o(t)$ and sketch it wrt. time.