

EE210: Analog Electronics

Question Set 7

Instructor: Imon Mondal, imon@iitk.ac.in

1) Consider the circuit in Fig 1. $\mu_n C_{ox} = 0.2 \text{ mA/V}^2$, $I_0 = 1 \text{ mA}$, $V_{DD} = 6 \text{ V}$, $R_1 = R_2 = 2 \text{ k}\Omega$, $V_{tn} = 1 \text{ V}$.

 


Figure 1: Question 1.

- Size M_1 and M_2 such that M_1 is in saturation with a margin of 500 mV, and $g_{M1} = 1 \text{ mS}$.
- Find the incremental resistances r_1 and r_2 .
- Use the configuration to implement a common source amplifier.
- If you want to implement a CCCS, where and how will you apply the i/p and take the o/p?
- How is this config. different from a standard common gate config.?
- If you want to implement a VCVS having gain ≈ 1 while driving a load $R_L \approx 1 \text{ k}\Omega$ to $2 \text{ k}\Omega$, what will you do?

2) The circuit shown in Fig. 2 is used to generate a bias voltage $V_B = V_{tn} + V_{ov}$. If we want to generate a bias voltage of $V_B = V_{tn} + 2V_{ov}$, how will you change the circuit without changing the I_0 ?

3) $I_0 = 1 \text{ mA}$, $(W/L)_1 = 10$, $\mu_n C_{ox} = 200 \mu\text{A/V}^2$, $\mu_p C_{ox} = 100 \mu\text{A/V}^2$ $(W/L)_2 = 20$, $V_{DD} = 5 \text{ V}$

 


Figure 2: Question 2.

 


Figure 3: Question 3

- Find the quiescent current through M_1 and M_2 .
- Between M_1 and M_2 , what will you change to bias M_1 at the edge of saturation region?
- Among the four types of biasing schemes that you have learnt, which one is being used here to bias M_1 ?
 - Observe the drain, feedback at source.
 - Observe the drain, feedback at gate.
 - Observe the source, feedback at source.
 - Observe the drain, feedback at gate.

d) Find the maximum and minimum V_B required to keep both the transistors in saturation while maintaining the constraint of a minimum overdrive voltage of 100 mV?