

EE210A: Microelectronics I

Problem Set 3

Instructor: Imon Mondal, imon@iitk.ac.in

Assume $\mu_n C_{ox} = 200 \mu A/V^2$ and $V_{tn} = 1V$ for all transistors in the problem set.

1) : Consider $V_{DD} = 5V$, $W/L = 10$, and $R_L = 1k\Omega$.

Plot V_D with respect to V_B , when V_B is swept from 0 to 5V. Mark the points corresponding to the regions of operation in the plot.

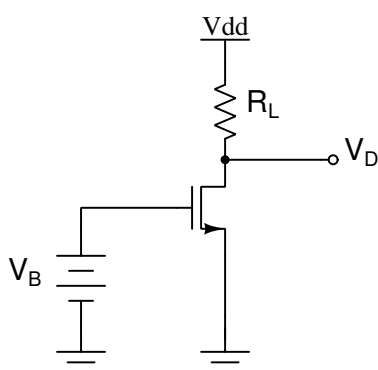


Figure 1: Problem 1.

2) : Consider the Fig. 2. $V_{DD} = 5V$, $R_L = 10k\Omega$.

a) : Find V_B and W/L of M1 for a small signal gain of -10 between v_i and v_o . Is the solution unique?

b) : If $v_i = V_p \sin(\omega_0 t)$, find V_B and W/L while ensuring maximum possible V_P for which M1 remains in saturation and away from cutoff (Use Q-point + incremental model for analysis), and ensuring a gain of -10 .

3) : Consider Fig. 3. $V_{DD} = 5V$, $(W/L)_1 = 10$, $(W/L)_2 = 5$, $V_B = 2V$, $R_1 = 2k\Omega$, $R_2 = 1k\Omega$.

a) : Find the small signal gain between v_i and v_{d1} , and between v_i and v_{d2} .

b) : If $v_i = V_p \sin(\omega_0 t)$, find the maximum V_p such that M1 remains in saturation and away from cutoff region of operation. (Use linear incremental

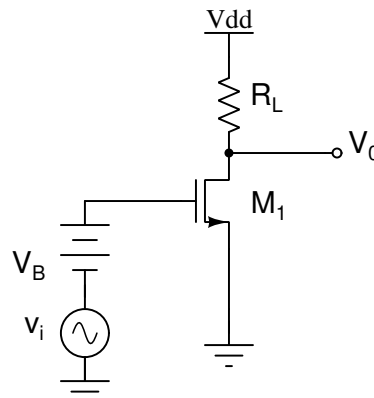


Figure 2: Problem 2.

analysis)

c) : If $v_i = V_p \sin(\omega_0 t)$, find the maximum V_p such that both M1 and M2 remain in saturation and away from cutoff region of operation. (Use linear incremental analysis)

d) : Sketch the waveforms at the gates and the drains of M1 and M2 under these conditions. e) : If another common-source stage is cascaded to V_{D2} , comment on the maximum allowable amplitude of the input sinusoid with respect to the circuit shown in the figure.

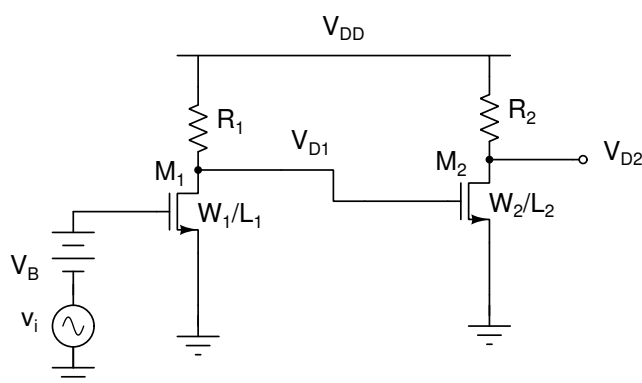


Figure 3: Problem 3.

4) : Sketch the incremental (small-signal) Norton's equivalent network for the following configurations. Replace the transistor with its small signal model, assuming saturation region of operation. (Note that the input v_i has not been applied between the gate and source. Make necessary adjust-

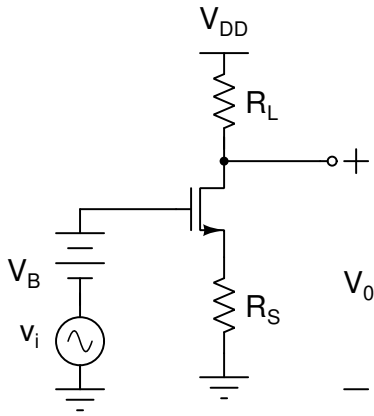


Figure 4: Problem. 4a

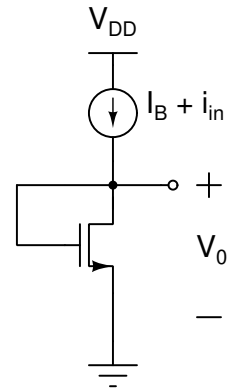


Figure 6: Problem. 4c

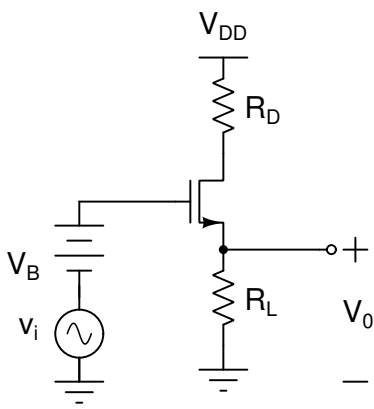


Figure 5: Problem. 4b

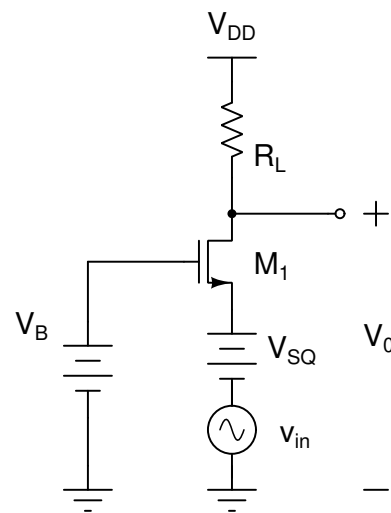


Figure 7: Problem. 4d

ments in your KCL equations.)

5) : Consider the Fig. 8. $V_{DD}=3V$, $R_L = 1k\Omega$, $(W/L) = 10$.

- a) : Find V_B such that the quiescent $V_0=0.5V$.
- b) : What is the small signal gain between v_i and v_o ?
- c) : If $v_i = V_p \sin(\omega_0 t)$, what is the maximum V_p that you can apply while ensuring $M1$ remains in the saturation and away from the cutoff. (Use quiescent + incremental model for analysis)

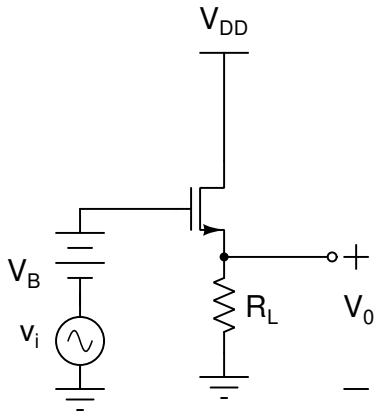


Figure 8: Problem 5.