

EE210A: Microelectronics I

Problem Set 6

Instructor: Imon Mondal, imon@iitk.ac.in

1) Consider the circuit in Fig 1. $\mu_n C_{ox} = 0.2 \text{ mA/V}^2$, $I_0 = 1 \text{ mA}$, $V_{DD} = 6 \text{ V}$, $R_1 = R_2 = 3 \text{ k}\Omega$, $V_{tn} = 1 \text{ V}$. Assume $g_{mb} = 0.2 g_m$. (Neglect channel length modulation)

- Size M_1 and M_2 such that M_1 is in saturation with a margin of 500 mV, and $g_{M1} = 1 \text{ mS}$.
- Find the incremental resistances r_1 and r_2 .
- Use the configuration to implement a common source amplifier.
- If you want to implement a CCCS, where and how will you apply the i/p and take the o/p?
- How is this config. different from a standard common gate config.?
- If you want to implement a VCVS having gain ≈ 0.9 while driving a load $R_L \approx 1 \text{ k}\Omega$ to $2 \text{ k}\Omega$, what will you do?

 


Figure 1: Problem 1.

2) The circuit shown in Fig. 2 is used to generate a bias voltage $V_B = V_{tn} + V_{ov}$. If we want to generate a bias voltage of $V_B = V_{tn} + 2V_{ov}$, how will you change the circuit?

3) Consider the current mirror in Fig. 3. $I_0 = 100 \mu\text{A}$, $(W/L)_1 = (W/L)_2 = (W/L)_3 = (W/L)_4 = 10$ and $V_{tn} = 1 \text{ V}$. Neglect body effect. Also, consider $\mu_n C_{ox} = 0.2 \text{ mA/V}^2$ and $\lambda = 0.1 \text{ V}^{-1}$.

- Find V_{S3}, V_{S4}, V_{G3} . Who sets the voltages

 


Figure 2: Problem 2.

V_{S3} and V_{S4} ? (Neglect CLM for calculating Q-point)

- Find the incremental R_{out} .
- Find the minimum V_X while keeping all transistors in saturation.
- If V_X changes by 100 mV (while keeping M_4 is saturation) how much change in current will you observe through M_2 ?
- If V_X changes by 100 mV, how much change in V_{S4} will you observe?
- What will you do if you want to reduce V_{S3} and V_{S4} by 100 mV without affecting anything else?

 


Figure 3: Problem 3.

4) Consider the circuit in Fig. 4. The currents I_0 , and the transistors $M1 - M4$ are identical to that of Q3.

- a) : Is it possible to have $V_{Xmin} = 2V_{ov|M2,M4}$?
- b) : What must V_{G5} be to realize the condition in a)?
- c) : How will you size $M5$ to set this V_{G5} ?

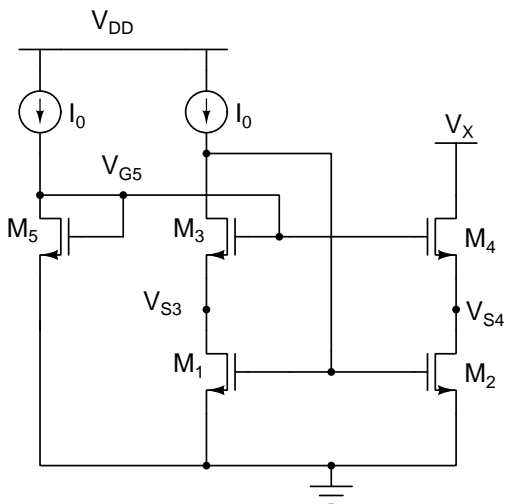


Figure 4: Problem 4.

5) Consider Fig. 5. $(W/L) = 10$ for all transistors, $V_{tn}=1V$, $\mu_n C_{ox}=200 \mu A/V^2$.

- a) : Assume $I_{DS2} = 1mA$. Find the incremental R_{out} .
- b) : How does this architecture fare with respect to the previous ones?

 


Figure 5: Problem 5.

6) Consider the Fig. 6. The amplifier in Q5. has been replaced by a common source stage. (Neglect channel length modulation for $M5$)

- a) : Size $M5$ such that $V_{DSM2} = V_{DSM1}$.
- b) : What is the gain of the common source stage?

c) : If you want to move the V_{DSM2} up or down, what will you change in the circuit?

d) : If I_0 changes to $I_0 + \Delta I$, what will be the total voltage at the drain of $M2$? (Neglect channel length modulation for this part).

 


Figure 6: Problem 6.