 


Home Assignment #2

① A designer decides to bias a transistor in the following manner. The transistor parameters are marked in the diagram.



② What is the region of operation?

③ Find V_o .

② A MOS transistor is biased in saturation region. The designer observes that the g_m of the transistor increases linearly with V_L .

⊛ Show a biasing scheme (with ideal voltage or current sources) which will lead to the above observation.

③ Show a biasing scheme if the designer observes that $g_m \propto \sqrt{V_L}$

④ A designer wants to increase the g_m of a transistor by 2x without changing the g_{ds} . Suggest a way of doing it. The transistor should be biased in saturation region of operation.

⑤ A MOSFET has the following parameters. $V_D = 2V$


$$M_{ox} \frac{W}{L} = 2mA/V^2 \quad V_{th} = 1V \quad \lambda = 0$$

Plot g_m and g_{ds} vs V_{gs}

for $0 < V_{gs} < 4V$.

⑥ A designer observes that the intrinsic gain (g_m/g_{ds}) decreases as she increases W/L . What is the biasing scheme that she is using? You can use ideal voltage and current sources if you find it necessary.

 7) Find the short-circuit currents for the following configurations.





(i) $Z = R$

(ii) $Z = 1/sC$

(iii) Z is a parallel combination of R and C

  (iv) Plot I_{sc} vs ω for $0 \leq \omega \leq \infty$ using Bode approximation



8

: Consider a two port network as discussed in the class. Assume $I_1 = 0$, and $I_2 = \alpha(V_1 - V_{th})^n / V_A^n$ for $V_1 > V_{th}$ where α , V_{th} and V_A are positive constants and $n \geq 2$ is a positive integer and $I_2 = 0$ for $V_1 < V_{th}$. Assume that a resistance R_L is connected to port 2.

a) : Find the incremental voltage gain between ports 1 and 2.

b) : Find the second and third harmonic distortion at the output if an input $V_{th} + V_{ov} + V_p \sin(\omega t)$ is applied at port 1, where $V_p < V_{ov}$ and $V_{ov} > 0$.

c) : For identical linear voltage gains (same HD1), comment on the strengths of the distortion components as you increase n .

d) : To achieve identical HD1, comment on the quiescent voltage requirements at port 1 as you increase n .